

7E7084

Roll No. 15EB3E021Total No of Pages: 3

7E7084

B. Tech. VII Sem. (Main / Back) Exam., Nov. – Dec. - 2018
 Electronics & Communication Engineering
 7EC5A VLSI Design

Time: 3 Hours

Maximum Marks: 80

Min. Passing Marks: 26

Instructions to Candidates:

Attempt any five questions, selecting one question from each unit. All questions carry equal marks. Schematic diagrams must be shown wherever necessary. Any data you feel missing suitably be assumed and stated clearly.

Units of quantities used/calculated must be stated clearly.

Use of following supporting material is permitted during examination. (Mentioned in form No. 205)

1. NIL2. NIL**UNIT- I**

Q.1 (a) What are different kinds of MOS transistors? Explain the structure and operation of MOS transistor. [8]

(b) The process parameters for an NMOS are - [8]

Oxide thickness = 500 \AA , Substrate doping $M_A = 10^{16}/\text{cm}^3$, Polysilicon gate doping $M_D = 10^{20}/\text{cm}^3$, Oxide interface fixed charge density = $2 \times 10^{10}/\text{cm}^3$.

Calculate the threshold voltage V_T .

OR

Q.1 (a) What are the different techniques of CMOS transistor fabrication? Explain one in detail. [8]

(b) Explain "Depletion mode MOSFET". [8]

[7E7084]

Page 1 of 3

[3320]

UNIT- II

Q.2 (a) Write short note on –

[8]

(i) Noise Margins

(ii) Pull-up to pull – down ratio for an NMOS inverter.

(b) Design a resistive load inverter with $R = 1k\Omega$ such that at $V_{OL} = 0.6V$. The enhancement type NMOS driver transistor has following parameters :

$$V_{DD} = 5V, V_T = 1V, \mu_n \cdot C_{ox} = 22\mu A/V^2 -$$

[8]

(i) Determine the aspect ratio

(ii) Determine Noise margins NM_L and NM_H .

OR

Q.2 (a) Derive β_n/β_p ratio of CMOS inverter.

[10]

(b) The NMOS device with $V_t = 0.7V$ has its source terminal grounded and a 1.3V is applied to gate. The device has $\mu_n \cdot C_{ox} = 100 mA/V^2$, $W = 10mm$, $L = 1mm$. Find the value of drain current for $V_D = 3V$.

[6]

UNIT- III

Q.3 (a) Realize the following expression using CMOS inverter –

[8]

(i) $AB + \overline{A} \overline{B}$

(ii) $\overline{A + BC + DE}$

(iii) $AB + BC + AC$

(iv) $A \odot B$

(b) What are DRC rules for layout? State any six DRC rules.

[8]

OR

- Q.3 (a) Draw the layout using Euler path for $y = \overline{(\Lambda + BC)(D + E)}$. [8]
- (b) Draw latch – up formation in CMOS inverter. [8]

UNIT- IV

- Q.4 (a) What is C^2 MOS logic? Draw logic circuit using it. What are advantages of such logic? [8]
- (b) Explain the working of SRAM cell and DRAM cell. [8]

OR

- Q.4 (a) Explain pre – charge and evaluation logic. [8]
- (b) Draw $y = \overline{(AB + C)}$ using Domino logic. [8]

UNIT- V

- Q.5 (a) Write VHDL Code for S – R flip flop and D-flip flop. [10]
- (b) List the advantages and limitations of VHDL. [6]

OR

- Q.5 (a) Write the difference between FPGA and custom design. [8]
- (b) Write the difference between first and back end design. [8]